

Output:

```
VCD info: dumpfile Gray_to_sevensegment.vcd opened for output.  
A=0 B=0 C=0 -> a=1 b=1 c=1 d=1 e=1 f=1 g=0  
A=0 B=0 C=1 -> a=0 b=1 c=1 d=0 e=0 f=0 g=0  
A=0 B=1 C=1 -> a=1 b=1 c=1 d=1 e=0 f=0 g=1  
A=0 B=1 C=0 -> a=0 b=1 c=0 d=1 e=1 f=0 g=1  
A=1 B=1 C=0 -> a=1 b=0 c=1 d=1 e=1 f=1 g=1  
A=1 B=1 C=1 -> a=1 b=1 c=1 d=0 e=0 f=0 g=1  
A=1 B=0 C=1 -> a=1 b=0 c=1 d=1 e=0 f=1 g=1  
A=1 B=0 C=0 -> a=1 b=1 c=1 d=0 e=0 f=1 g=0  
Gray_to_sevensegment_tb.v:42: $finish called at 80000 (1ps)
```

Waveform:

